

Marks	Particulars	CO1	CO2	CO3	CO4	L1	L2	L3	L4	L5	L6	Distribution
Test	Max Marks	08	46	06	-	20	34	06	-	-	-	

Q.No	Questions	Marks	COs	BT
PART - B				
1. a)	Derive the E.M.F equation of a transformer.	04	02	02
b)	A 600 KVA transformer has an efficiency of 92% at full-load, unity power factor and at half-load, 0.9 power factor. Determine its efficiency at 75% of full-load and 0.9 power factor.	06	03	03
2. a)	Explain the constructional details of core and shell type transformer.	05	02	01
b)	A single phase, 20 KVA transformer has 1000 primary turns and 2500 secondary turns. The net cross-sectional area of the core is 100 cm^2 . When the primary winding is connected to 500V, 50 Hz supply. Calculate the maximum value of the flux density in the core	05	02	02
3. a)	A coil of power factor 0.6 is in series with 100μF. When connected to a 50Hz supply, the potential difference (p.d) across the coil is equal to the p.d. across the capacitor. Find the resistance and inductance of the coil.	05	02	02
b)	Show that a pure inductance does not consume any power. Draw the waveforms of voltage, current and power, when a sinusoidal voltage is applied to a pure inductance.	05	02	02
4. a)	Define the following terms: i) Instantaneous value ii) Amplitude iii) Form factor and iv) Peak factor	04	01	01
b)	A current $i = 10 \sin(314t - 10^\circ)$ A produces a potential drop $V=220 \sin(314t+20^\circ)$ V in a circuit. Find the values of the passive elements, assuming a series combination of only two passive elements is supplied from a source.	06	02	02
5. a)	Derive an equation for the power consumed by an R-C series circuit. Draw the waveforms of voltage, current, and power.	05	02	01
b)	An inductive coil takes a current of 33.24 A from 230V, 50Hz supply. If the resistance of the coil is 6Ω. Calculate the inductance of the coil and the power taken by the coil.	05	02	02




Q.No	Questions	Marks	COS	BT
PART - A				
1.	Define voltage regulation of a transformer.	2	C02	L1
2.	A 11000 / 220V , 50Hz, 1-phase transformer takes a current of 20A, if the number of turns on the primary side is 1000. The primary and secondary currents are $I_1 = \dots$ and $I_2 = \dots$	2	C02	L2
3.	Mention the constant and variable losses in transformers, and also write the equation for the same.	2	C01	L1
4.	The current in a circuit is $(8 - j10)$ A, when the applied voltage is $(50 + j25)$ V . determine the impedance and power factor of the circuit.	2	C01	L2
5.	The equation for an alternating current is given by $i = 28.28 \sin(314t + 30^\circ)$ A. Find its r.m.s, frequency and phase angle	2	C02	L1

Basics of Electrical Engineering

Date	2nd July 2024	Maximum Marks	60	Course Code	EE123ATD	DURATION	II Semester	Improvement Test	Sem
Basics of Electrical Engineering									

Department of Electrical & Electronics Engineering

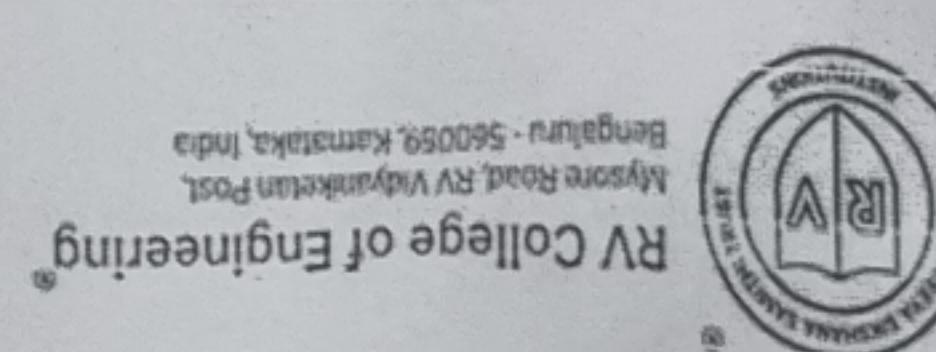RV College of Engineering
Mysore Road, RV Vidyashankar Post,
Bengaluru - 560059, Karnataka, India
Phone: 080-68188192
Email: rvice.edu.in
NBA Accredited (UG & PG)
www.rvice.edu.in



SCHMEE AND SOLUTION

RV College of Engineering



Bengaluru - 560059, Karnataka, India

Department of Electrical & Electronics Engineering

04

Marks

Tel: 080-6818
www.rvee.org
hod.eee@rvee.org

Determine the resistance and inductance of the load per phase, the total reactive power and total apparent power.	6	2	3
Prove that, the readings of the wattmeter's are in terms of $\cos(30 + \phi)$ and $\cos(30 - \phi)$ while measuring the power of a three-phase circuit. Mention the status of two wattmeter's at power factors: 1, 0.5 and 0 respectively.	4	3	2
b) Input power to a three-phase circuit was measured by two wattmeter method. The readings were 3kW and 1.5kW. Determine the total power consumed and the power factor of the balanced three phase circuit.	9	21	20

BT-Blooms Taxonomy, CO-Course Outcomes, M-Marks

Marks	Particulars	CO1	CO2	CO3	CO4	L1	L2	L3	L4	L5	L6	Test Marks	Max Marks	Distribution
		-	-	-	-	17	33	-	-	-	-	9	21	20

le

um

Quiz-3	Test-3	Total
5	5	10

CIE-2

LAB

Unit-3



RV College of Engineering®
Mysore Road, RV Vidyanketan Post,
Bengaluru - 560059, Karnataka, India

Quiz-1	Total	Unit-2	Quiz-2	Total	Unit-3	Quiz-3	Total	Unit-3	Quiz-2	Total	Unit-1	Quiz-1
T1	T2	T3	A1	A2	A3	LAB	Ass / EL	CIE	A/S	CIE	Ass / EL	Quiz-1
33	33	33	33	33	33	33	33	33	33	33	33	33

NBA Accredited (UG & PG)

hod.ee@rvce.edu.in
www.rvce.edu.in
Tel: 080-68188192

Department of Electrical & Electronics Engineering

Basics of Electrical Engineering

Date	19 th June 2024	Maximum Marks	50
Course Code	22ES24D	Duration	90 Mins
Sem	II Semester	CIE -2	


Basics of Electrical Engineering

Q.No	CIE - 2	Marks	COs	BT
1. a)	Derive expressions for Effective and Average value of an alternating quantity.	4	2	2
b)	An alternating current varying sinusoidally with a frequency of 50 Hz has an RMS value of 20 A. Write down the equation for the instantaneous value and find this value (a) 0.0025 second (b) 0.0125 second after passing through a positive maximum value. At what time, measured from a positive maximum value, will the instantaneous current be 14.14 A?	6	2	3
2. a)	Prove that in a series RL Circuit, Power consumed is $P = VI\cos\phi$ with all relevant equations, phasor diagram and Graphical representation.	5	2	3
b)	A current of 5 A flows through a non-inductive resistance in series with a choking coil when supplied at 250-V, 50-Hz. If the voltage across the resistance is 125 V and across the coil 200 V, calculate (a) impedance, reactance and resistance of the coil (b) the power absorbed by the coil and (c) the total power. Draw the vector diagram.	5	3	3
3. a)	A three-phase delta connected motor operating on a 400 V supply is delivering 25 HP at an efficiency of 0.87 and power factor of 0.42. Calculate the line current, phase current and the readings of two-watt meters connected to measure the input. Assume, 1hp=746 w.	6	3	3
b)	Explain the advantages of 3 phase circuits over single phase circuits.	4	1	2
4. a)	Arrive at the Voltage and Current expressions for 2 types of connections of a 3-phase circuit.	5	1	2
b)	A balanced, three phase, star connected load is fed from a 400V, three phase, 50Hz supply. The current per phase is 25 A(lagging) and the total active power absorbed by the load is 13.856 kW.	5	3	3



Academic year 2023-2024 (EVEN Sem)

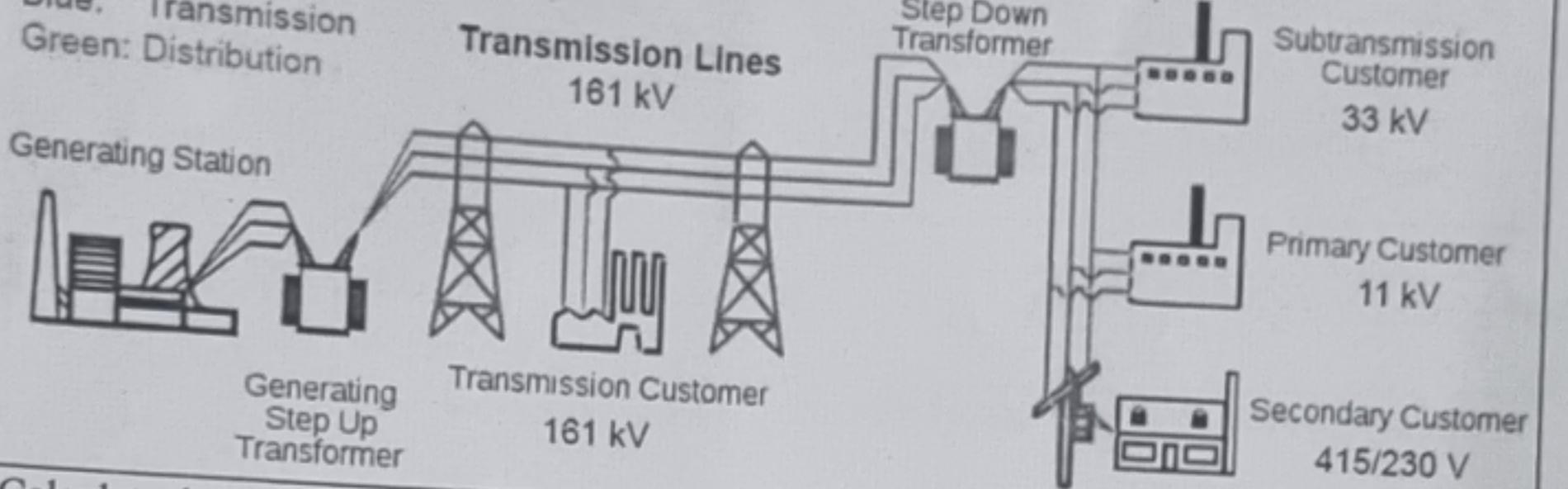Colour Key:
Black: Generation
Blue: Transmission
Green: Distribution



- b) Calculate the electric bill at the end of a month of 30 days at Rs.2.00 per unit if 6 lamps of 40 watt each burn for 8 hours per day, an electric iron of 1 kW is used for 2 hours per day and 4 fans of 50 watt each are used for 10 hours per day.

6 4

Name of the Appliance	Power Rating (W)	Avg. Daily Usage Hrs	No. of Appliances	Daily Energy Required (Wh)
lamps	40	8	6	1920
electric	1kw	2	1	2000
fan	50	10	4	2000
Total Energy				5920Wh


$$\text{Total energy consumed per day } E_{\text{total}} = E_1 + E_2 + E_3 \\ = 1920 + 2000 + 2000 = 5920 \text{ Wh}$$

5.920 kWh or units

$$\text{Total energy consumed per month} = 30 \times E_{\text{total}} \\ = 30 \times 5.92 = 177.60 \text{ kWh or 177.60 units}$$

$$\text{Bill for one month} = \text{Rate/unit} \times \text{units} = (\text{Rs.2.00/unit}) \times (177.60 \text{ units}) \\ = \text{Rs.}355.20$$

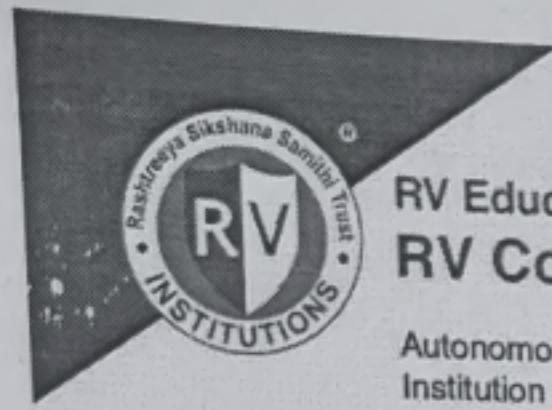So the electric bill at the end of a month will be **Rs.355.20**



RV Educational Institutions®
RV College of Engineering®

Autonomous
Institution Affiliated
to Visvesvaraya
Technological
University, Belagavi

Approved by AICTE,
New Delhi

NBA Accredited (UG & PG)

hod.ee@rvce.edu.in
www.rvce.edu.in
Tel: 080-68188192



Go, change the world

Academic year 2023-2024 (EVEN Sem)

	5. Electrical hazards include exposed energized parts and unguarded electrical equipment which may become energized unexpectedly. Such equipment always carries warning signs like "Shock Risk". 6. Always use appropriate insulated rubber gloves and goggles while working on any branch circuit or any other electrical circuit. 7. Never try repairing energized equipment. Always check that it is de-energized first by using a tester. 8. Never use an aluminum or steel ladder if you are working on any receptacle at height in your home. An electrical surge will ground you and the whole electric current will pass through your body. Use a bamboo, wooden or a fiberglass ladder instead.		
b)	What is the necessity of earthing the electrical appliances? Explain with diagram pl earthing. Necessity of Earthing: 1. To protect the operating personnel from danger of shock in case they come in contact with the charged frame due to defective insulation. 2. To maintain the line voltage constant under unbalanced load condition. 3. Protection of the equipments 4. Protection of large buildings and all machines fed from overhead lines against lightning.	6	3
5a)	Explain the concept of power transmission and distribution through block diagrams.	4	2



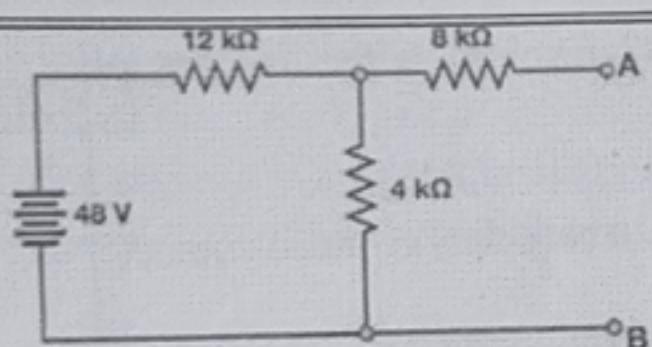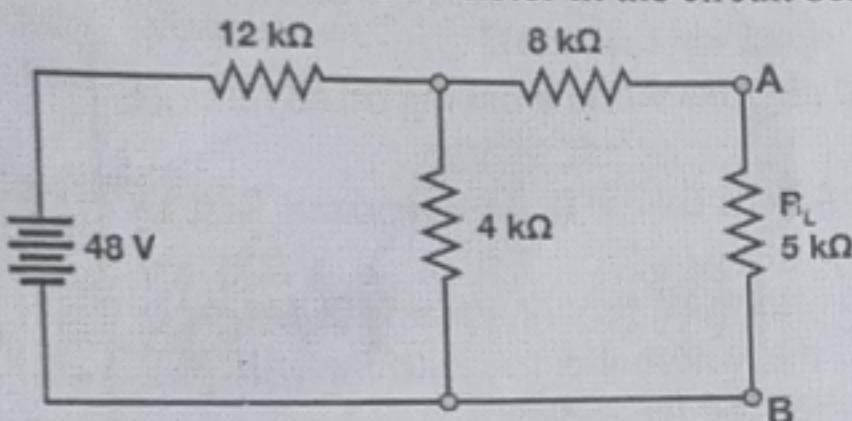- 3a) Using Thevenin's Theorem find V_{TH} , R_{TH} and the load current I_L flowing through and load voltage across the load resistor in the circuit below.



Remove the $5\text{ k}\Omega$ from the circuit. Measure the open-circuit voltage. This will give you the

Thevenin's voltage (V_{TH}). 0.75 mA

$$I = \frac{V}{R} = \frac{48}{12 + 4} = 3\text{ mA}$$

Thevenin's Resistance R_{TH} calculated as follows:



$$8\text{ k}\Omega + (4\text{ k}\Omega \parallel 12\text{ k}\Omega)$$

$$R_{TH} = 8\text{ k}\Omega + [(4\text{ k}\Omega \times 12\text{ k}\Omega) / (4\text{ k}\Omega + 12\text{ k}\Omega)]$$

$$R_{TH} = 8\text{ k}\Omega + 3\text{ k}\Omega$$

$$R_{TH} = 11\text{ k}\Omega$$

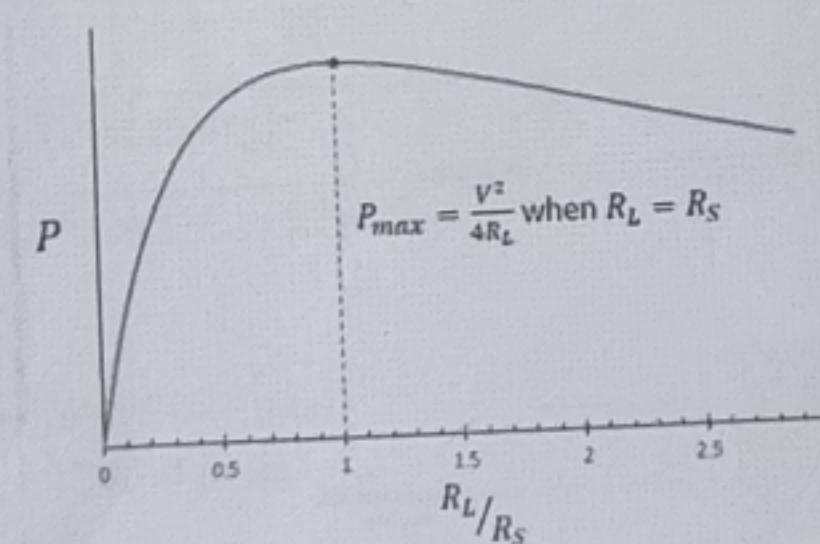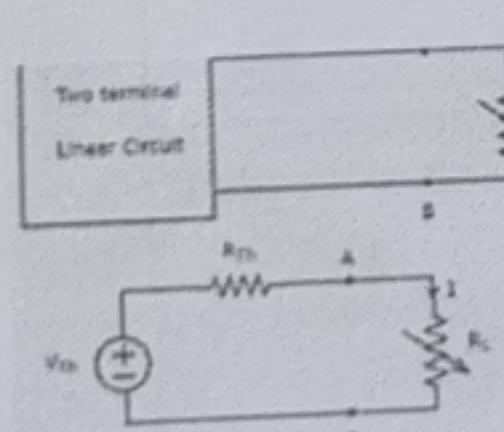- b) State and prove Maximum power transfer theorem.



The maximum power transfer theorem states that the power delivered to the load resistor is maximized when the load resistance is equal to the series resistance. This can be calculated by taking the derivative of the power equation with respect to the load resistance and calculating the critical point.

- 4a) Mention any eight precautions against Electric Shock.


1. The first step of electrical safety, avoid water at all times when working with electricity. Never touch or try repairing any electrical equipment or circuits with wet hands. It increases the conductivity of the electric current.
2. Never use equipment with frayed cords, damaged insulation, or broken plugs.
3. If you are working on any receptacle at your home then always turn off the mains. It is also a good idea to put up a sign on the service panel so that nobody turns the main switch ON by accident.
4. Always use insulated tools while working.

5 3

5 2

4 3

57	58	59	60	Final		
T1	T2	T3	A1	A2	A3	Total
Quiz-1	Quiz-2	Quiz-1	Quiz-2	Unit-1	Unit-2	Total
43	42	44	46	45	48	50
43	42	46	45	48	49	50
43	42	46	45	48	49	50
43	42	46	45	48	49	50
43	42	46	45	48	49	50

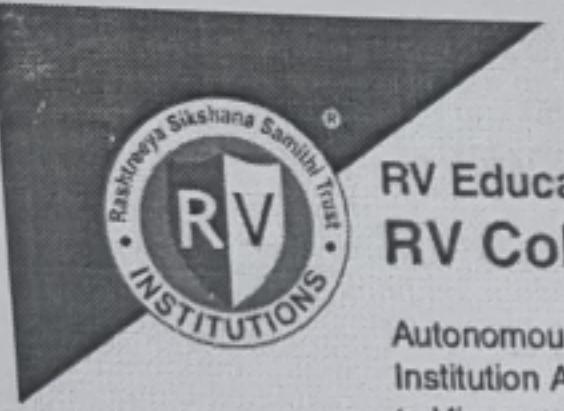

RV Educational Institutions®
RV College of Engineering®

Autonomous
Institution Affiliated
to Visvesvaraya
Technological
University, Belagavi

Approved by AICTE,
New Delhi

Academic year 2023-2024 (EVEN Sem)


Go, change the world

hod.ee@rvce.edu.in
www.rvce.edu.in
Tel: 080-68188192

Final Art	Quiz-1 Total	Quiz-1 Unit-1	Quiz-2 Total	Quiz-2 Unit-2	T1	T2	T3	A1	A2
943	0926	0526	0742	0733	45	48	42	43	44
944	0926	0526	0742	0733	45	48	42	43	44
945	0926	0526	0742	0733	45	48	42	43	44
946	0926	0526	0742	0733	45	48	42	43	44

2a)

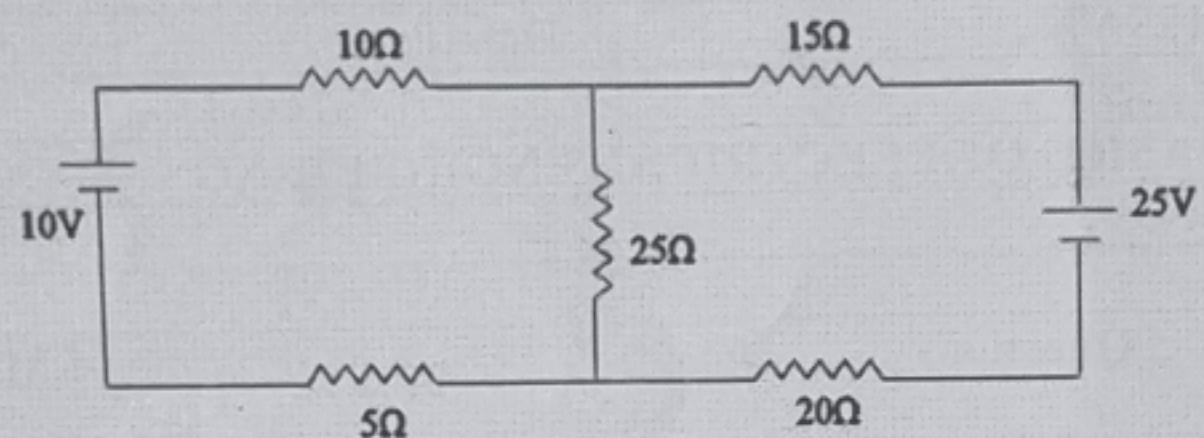Calculate the branch current in 15Ω resistor by applying Kirchhoff's law



5

2

Consider the loop BCDEB and Apply KVL in CLK wise direction

$$15I_1 - 25 + 20I_2 + 25\{I_1 + I_2\} = 0$$

$$15I_2 - 25 + 20I_1 + 25\{I_1 + I_2\} = 0$$

$$15I_2 - 25 + 20I_1 + 25I_1 + 25I_2 = 0$$

$$25I_1 + 60I_2 - 25 = 0$$


$$25I_1 + 60I_2 = 25 \dots\dots\dots(2)$$

$$I_2 = 0.42 \text{ Amps.}$$

Current in 15Ω resistor is 0.42Amps.

b)

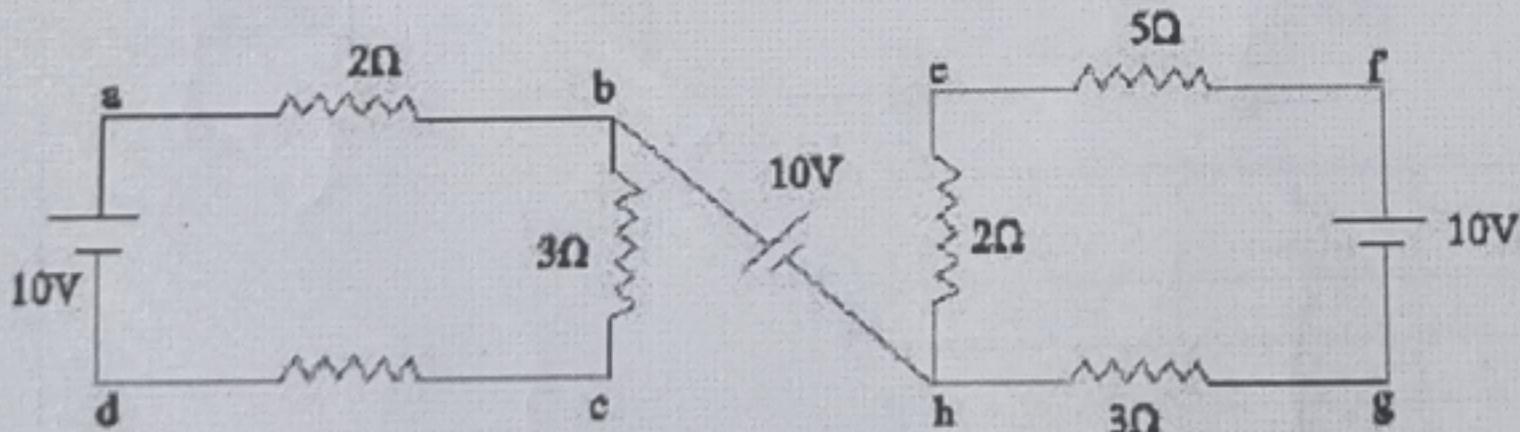For the Circuit shown below determine voltages V_{df} .



5

2

Apply KVL to loop abcd

$$10 - 2I_1 - 3I_1 - 5I_1 = 0$$

$$-10I_1 = -10$$


$$I_1 = 1 \text{ Amps}$$

Apply KVL to loop efghe

$$5I_2 - 10 + 3I_2 + 2I_2 = 0$$

$$10I_2 = 10$$

$$I_2 = 1 \text{ Amps}$$

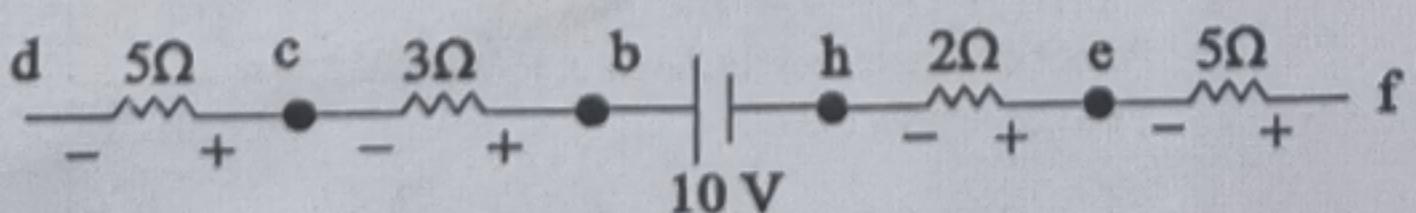

$$V_{df} = -5(I_1 - 3I_1 + 10 + 2I_2 + 5I_2)$$

$$V_{df} = -5 - 3 + 10 + 2 + 5$$

$$V_{df} = 9 \text{ Volts.}$$

$$V_{df} = -9 \text{ Volts} [\because \text{because - sign on d side + on f side}]$$

1	2
1	2
3	3

Go, change the world



RV Educational Institutions®
RV College of Engineering®

Autonomous
Institution Affiliated
to Visvesvaraya
Technological
University, Belagavi

Approved by AICTE,
New Delhi

Academic year 2023-2024 (EVEN Sem)

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

Date	13/05/24	Maximum Marks	50
Course Code	EE123AT	Duration	90 Min
Sem	2 nd sem	Test-1	
COURSE NAME: BASICS OF ELECTRICAL ENGINEERING			

SL No	Questions	Marks	CO																																
1a)	<p>Find the equivalent resistance of the circuit shown . Find the voltage drop over, current through, and power dissipated by each resistor.</p>	5	2																																
sol	<table border="1"> <thead> <tr> <th>Resistor (Ω)</th> <th>V (Volts)</th> <th>I (Amps)</th> <th>P (Watts)</th> </tr> </thead> <tbody> <tr> <td>16</td> <td>960</td> <td>60</td> <td>57600</td> </tr> <tr> <td>20</td> <td>240</td> <td>12</td> <td>2880</td> </tr> <tr> <td>3</td> <td>144</td> <td>48</td> <td>6912</td> </tr> <tr> <td>12</td> <td>96</td> <td>8</td> <td>768</td> </tr> <tr> <td>6</td> <td>96</td> <td>16</td> <td>1536</td> </tr> <tr> <td>4</td> <td>96</td> <td>24</td> <td>2304</td> </tr> <tr> <td>20</td> <td>1200</td> <td>60</td> <td>72000</td> </tr> </tbody> </table>	Resistor (Ω)	V (Volts)	I (Amps)	P (Watts)	16	960	60	57600	20	240	12	2880	3	144	48	6912	12	96	8	768	6	96	16	1536	4	96	24	2304	20	1200	60	72000		
Resistor (Ω)	V (Volts)	I (Amps)	P (Watts)																																
16	960	60	57600																																
20	240	12	2880																																
3	144	48	6912																																
12	96	8	768																																
6	96	16	1536																																
4	96	24	2304																																
20	1200	60	72000																																
b)	<p>A 100W, 200V bulb is put in series with a 60W bulb across a supply. What will be the current drawn? What will be the voltage across the 60W bulb? What will be the supply voltage?</p> <p>Power dissipated in the first bulb, $P_1 = V_1 I$ Current, $I = P_1 / V_1 = 100/200 = 0.5 \text{ A}$ Power dissipated in the second bulb, $P_2 = V_2 I$ Voltage across the 60 W bulb,</p> $P_2 = \frac{P_2}{I} = \frac{60}{0.5} = 120V$ <p>The supply voltage, $V = V_1 + V_2 = 200 + 120$ $V = 320V$</p> <p>The supply voltage, $V = 320 \text{ V}$.</p>	5	2																																