

PRINCIPLES OF ELECTRONICS ENGINEERING

Tutorial –3

1. Simplify the following logic expressions using Boolean postulates and theorems. Realize these expressions using basic gates.

(a)
$$Y = \overline{((\overline{AB} + ABC) + A(B + A\overline{B}))}$$

(b)
$$Y = AB + \overline{(AC)} + ABC(AB + C)$$

(c)
$$Y = \overline{AB}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + \overline{A}\overline{B}C$$

(d)
$$Y = (A + \overline{B} + C) \cdot (\overline{A} + \overline{B} + \overline{C}) \cdot (\overline{A} + B)$$

(e)
$$Y = AB + \overline{A}C + \overline{B}C$$

(f)
$$Y = \overline{[(\overline{(A + B)} \cdot (\overline{CD})) + E + \overline{F}]}$$

2. Realize the X-OR function using:

- (a). Only NAND gates
(b). Only NOR gates

3. Realize half adder using:

- (a). Only NAND gates
(b). Only NOR gates

4. A logic circuit has three inputs A, B and C and two outputs X and Y. The first output X is at logic 1, when two or more of the inputs are at logic 1. The second output Y is at logic 1, when only one of the inputs is at logic 1. Write the truth table, logic expressions for X and Y and realize the logic circuits using **NAND** gates only.

5. A logic circuit has four inputs A, B, C & D and three outputs X, Y and Z. The first output X is at logic 1 when any two inputs are at logic 1. The second output Y is at logic 1 when only one of the inputs is at logic 1. The third output is at logic 1 when three or more inputs are at logic 1. Write the truth table, logic expressions for X, Y and Z and realize the logic circuits using **NOR** gates only.

6. Simplify the given Boolean expression using k map.

a) $F(W,X,Y,Z) = \sum m(0,2,3,7,8,11,14,15)$

b) $F(A, B,C,D) = \sum m(0,2,5,6,7,8,10,13,15)$
